

Semiconductor Sensors:

Ch5: Temperatures Sensors Cont.

Lecturer: Dr. Navid Alaei-Sheini

Assistant Professor of Electrical Engineering
Shahid Chamran University of Ahvaz

روش ۱: استفاده از یک حسگر اضافی

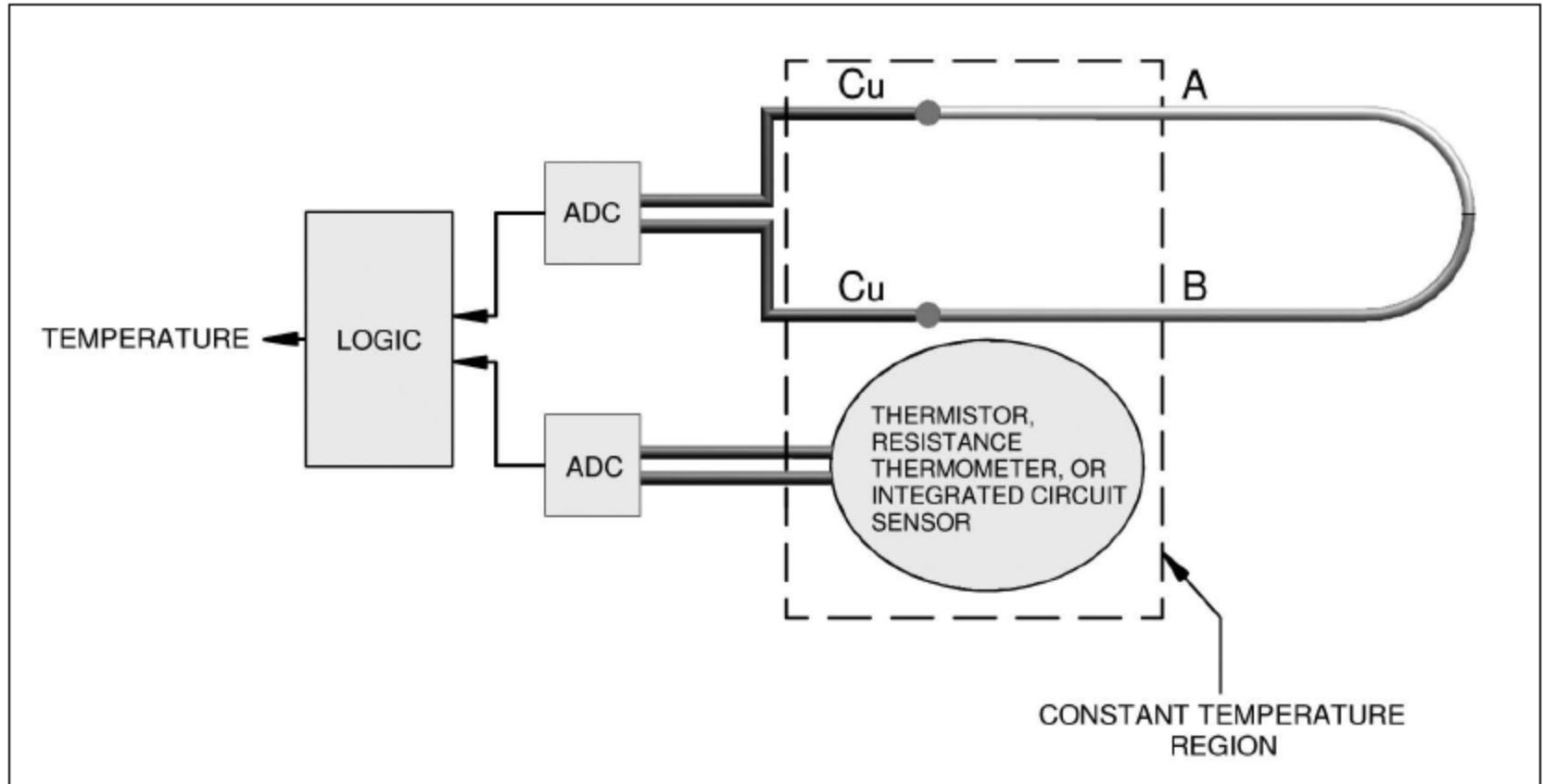


Figure 3-3. Computational Reference Junction Compensation


روش ۲: استفاده از مدارهای مجتمع خاص

Monolithic Thermocouple Amplifiers with Cold Junction Compensation

AD594/AD595

FEATURES

- Pretrimmed for Type J (AD594) or Type K (AD595) Thermocouples
- Can Be Used with Type T Thermocouple Inputs
- Low Impedance Voltage Output: 10 mV/°C
- Built-In Ice Point Compensation
- Wide Power Supply Range: +5 V to ±15 V
- Low Power: <1 mW typical
- Thermocouple Failure Alarm
- Laser Wafer Trimmed to 1°C Calibration Accuracy
- Setpoint Mode Operation
- Self-Contained Celsius Thermometer Operation
- High Impedance Differential Input
- Side-Brazed DIP or Low Cost Cerdip

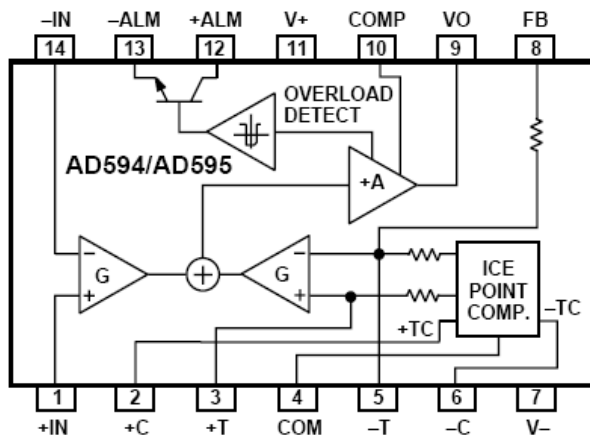

The temperature sensitivity of silicon integrated circuit transistors is quite predictable and repeatable. This sensitivity is exploited in the AD594/AD595 to produce a temperature related voltage to compensate the reference of “cold” junction of a thermocouple as shown in Figure 16.

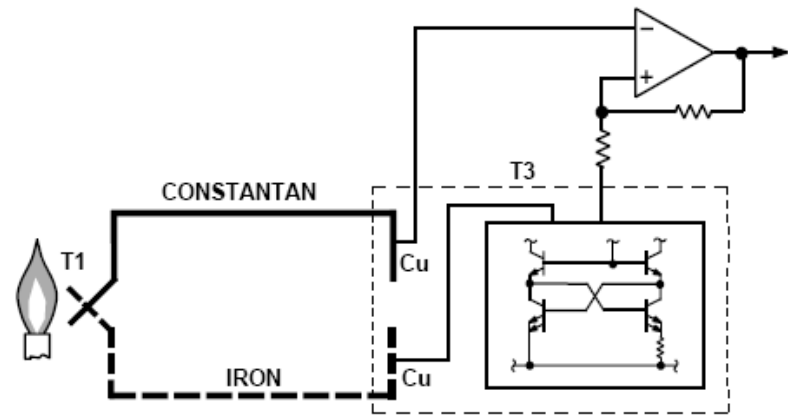


Figure 16. Connecting Isothermal Junctions

AD594/AD595 استفاده از مدارهای مجتمع

Table I. Output Voltage vs. Thermocouple Temperature (Ambient +25°C, $V_S = -5\text{ V}, +15\text{ V}$)

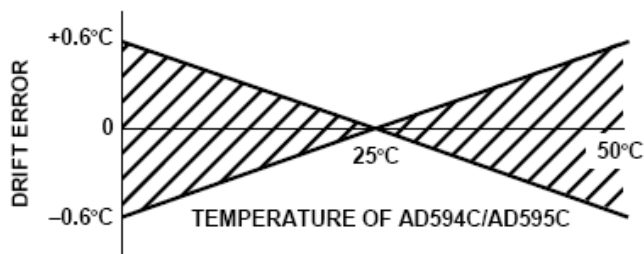


Figure 8. Drift Error vs. Temperature

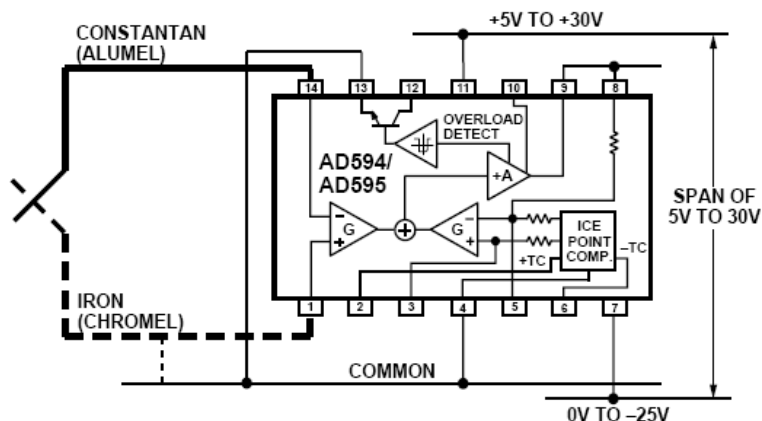


Figure 2. Dual Supply Operation

Thermocouple Temperature °C	Type J Voltage mV	AD594 Output mV	Type K Voltage mV	AD595 Output mV
-200	-7.890	-1523	-5.891	-1454
-180	-7.402	-1428	-5.550	-1370
-160	-6.821	-1316	-5.141	-1269
-140	-6.159	-1188	-4.669	-1152
-120	-5.426	-1046	-4.138	-1021
-100	-4.632	-893	-3.553	-876
-80	-3.785	-729	-2.920	-719
-60	-2.892	-556	-2.243	-552
-40	-1.960	-376	-1.527	-375
-20	-0.995	-189	-0.777	-189
-10	-0.501	-94	-0.392	-94
0	0	3.1	0	2.7
10	0.507	101	0.397	101
20	1.019	200	0.798	200
25	1.277	250	1.000	250
30	1.536	300	1.203	300
40	2.058	401	1.611	401
50	2.585	503	2.022	503
60	3.115	606	2.436	605
80	4.186	813	3.266	810
100	5.268	1022	4.095	1015
120	6.350	1233	4.910	1210

AD594/AD595 استفاده از مدارهای مجتمع

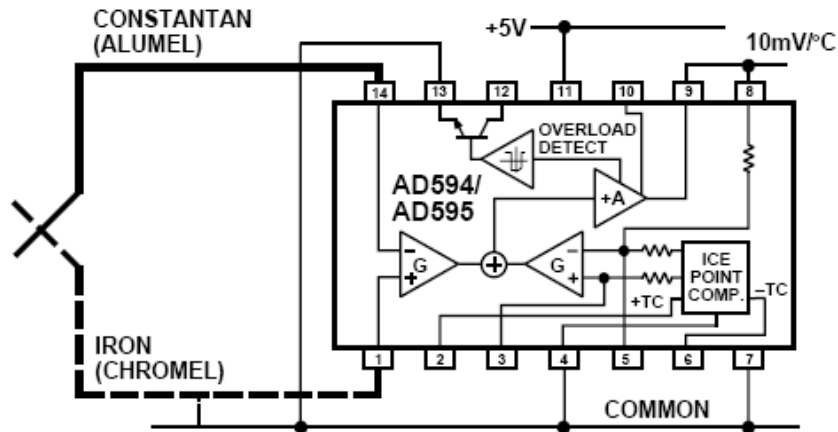


Figure 1. Basic Connection, Single Supply Operation


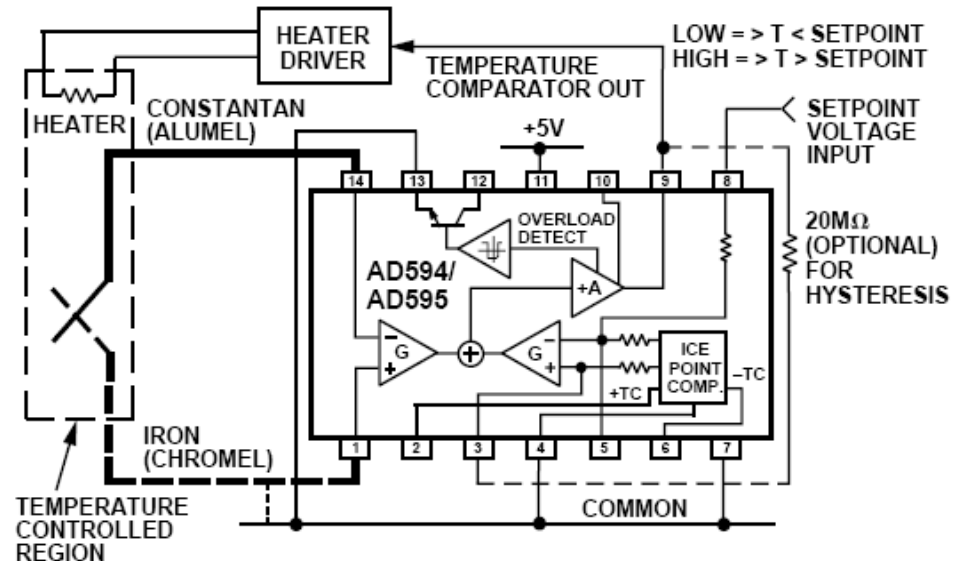



Figure 9. Setpoint Controller

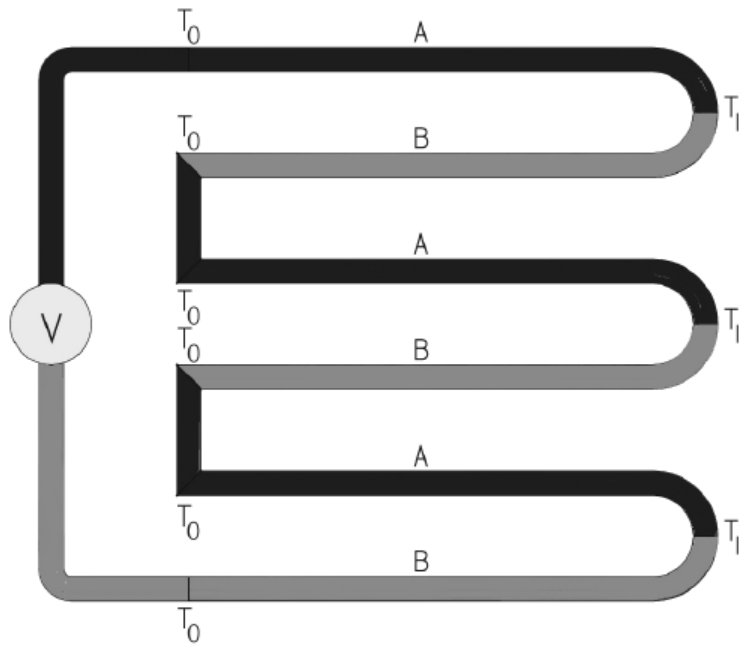Hysteresis can be introduced by injecting a current into the positive input of the feedback amplifier when the output is toggled high. With an AD594 about 200 nA into the +T terminal provides 1°C of hysteresis.



Thermocouples Wired in Series

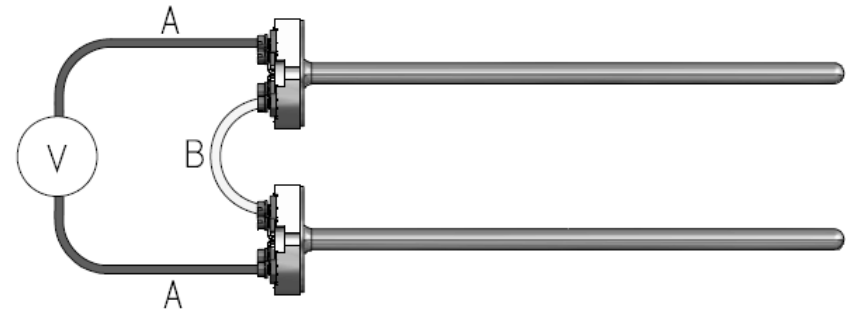This configuration, called a *thermopile*, may be used to obtain a larger signal than would be obtained with the normal single thermocouple arrangement.



Two Thermocouples Configured for Differential Measurements

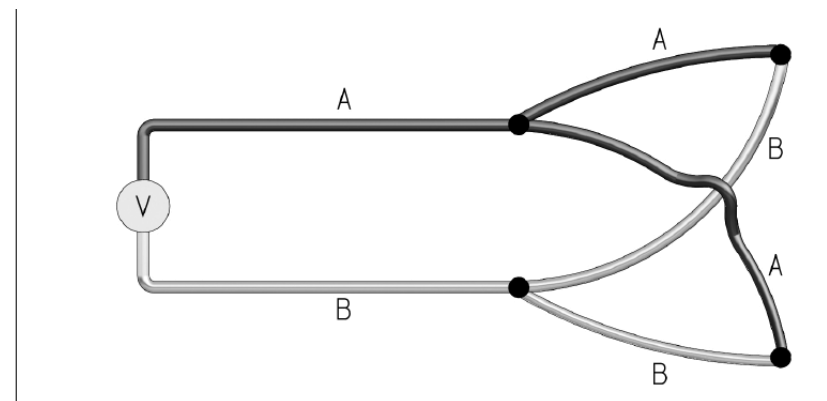


Figure 2-12. Thermocouples Wired in Parallel

$$E_T = \frac{\sum_1}{\sum_1 + \sum_2 + \dots + \sum_n} E_1 + \frac{\sum_{1_2}}{\sum_1 + \sum_2 + \dots + \sum_n} E_2 + \dots$$

where

- E_T = total emf from the circuit
- Σ_i = $1/R_i$ = electrical conductance of thermocouple I
- E_i = emf from thermocouple I


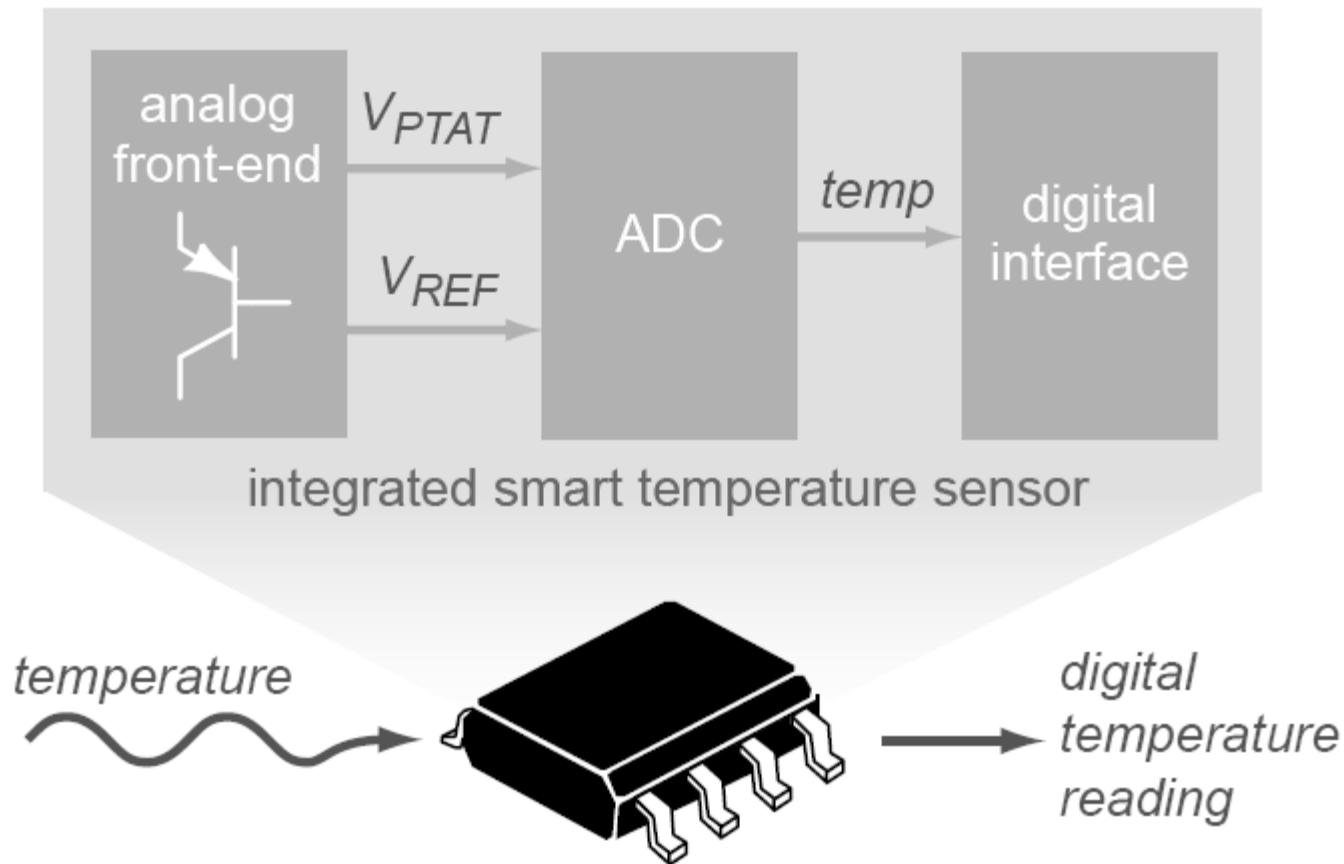
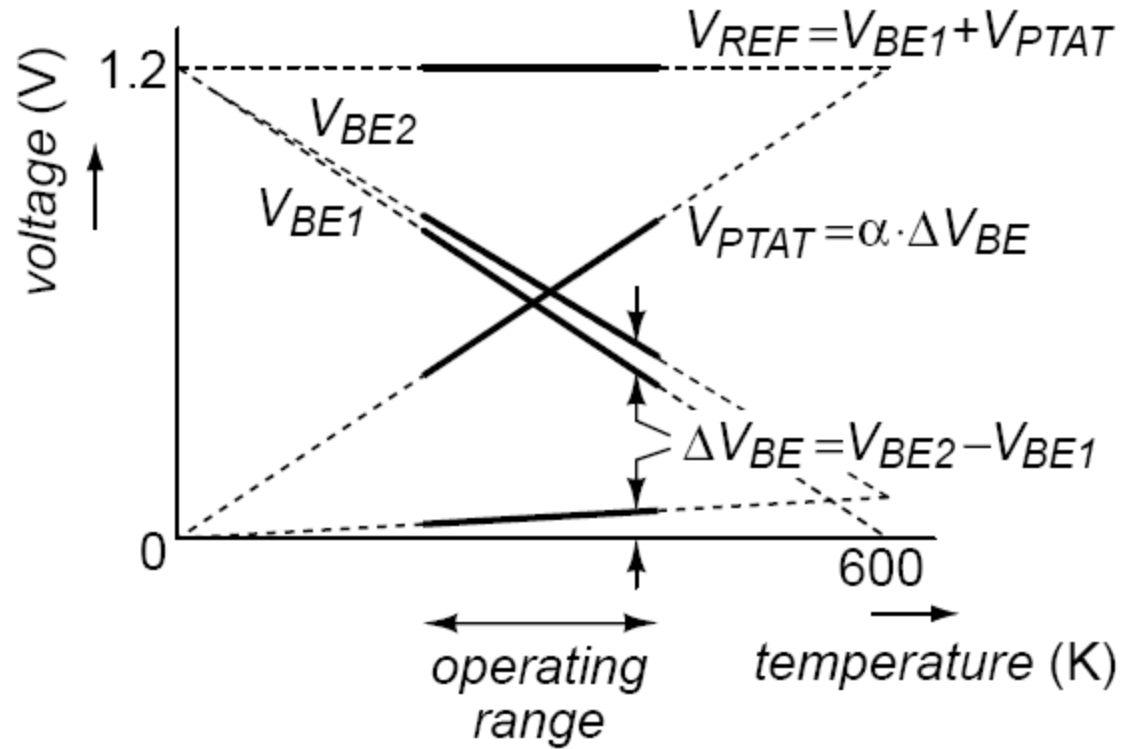


Figure 1.1. Block diagram of an integrated smart temperature sensor.

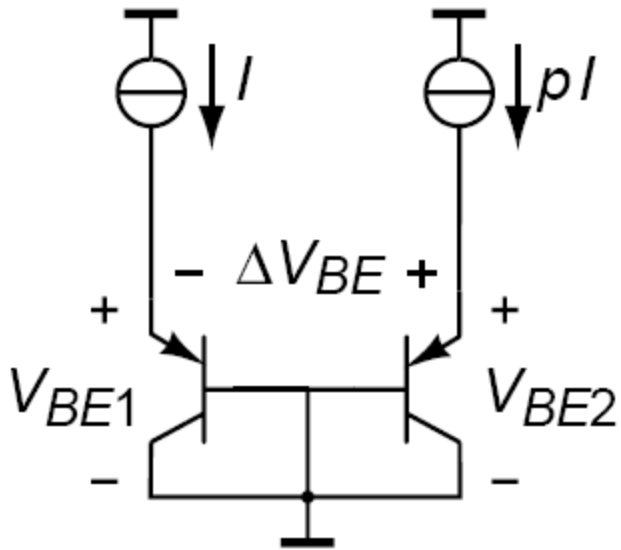

Proportional to Absolute Temperature (PTAT)

If an external voltage V is applied to a p-n junction, the balance between the drift and diffusion currents is disturbed:

$$n_{p-side} = n_{p0} \exp\left(\frac{qV}{kT}\right), \quad n_{p0} = \frac{n_i^2}{N_a}, \quad p_{n0} = \frac{n_i^2}{N_d},$$

$$p_{n-side} = p_{n0} \exp\left(\frac{qV}{kT}\right)$$


$$I_D = \frac{qAD_n(n_{p-side} - n_{p0})}{L_n} + \frac{qAD_p(p_{n-side} - p_{n0})}{L_p}$$

$$I_D = I_S \left(\exp\left(\frac{qV}{kT}\right) - 1 \right)$$

$$I_S = \frac{qAD_n n_{p0}}{L_n} + \frac{qAD_p p_{n0}}{L_p}$$

For forward-bias voltages $V \gg kT/q$,
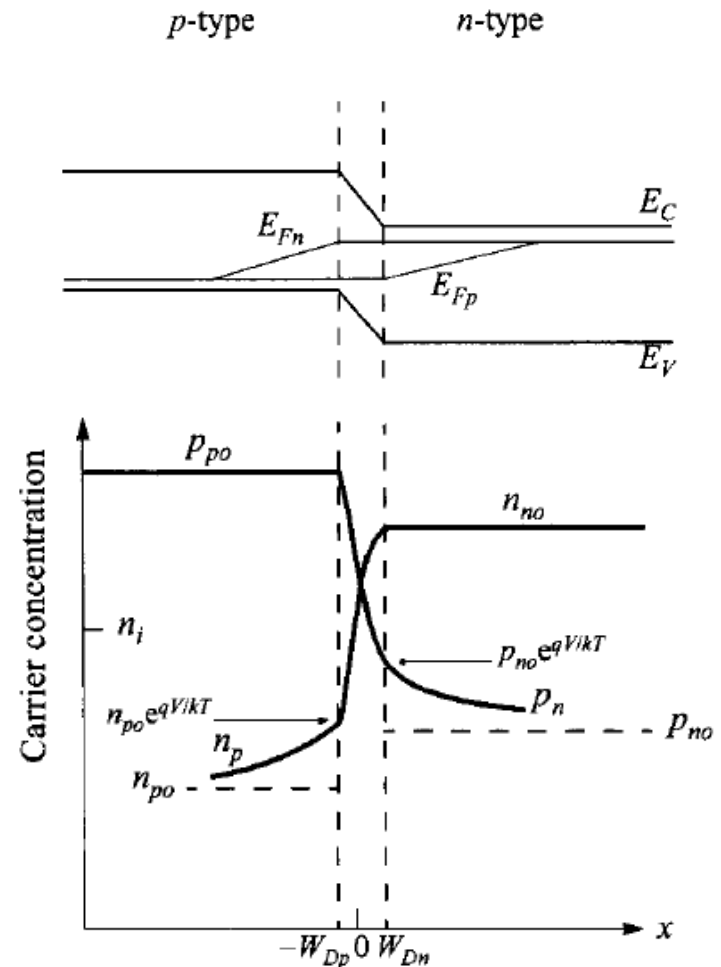
$$V = \frac{kT}{q} \ln\left(\frac{I}{I_S}\right)$$




S.M Sze and K. Neg, "Physics of semiconductors", 2006.

For forward-bias voltages $V \gg kT/q$,

$$V = \frac{kT}{q} \ln \left(\frac{I}{I_S} \right)$$

If two bias currents I_1 and $I_2 = pI_1$ are successively applied to a diode,
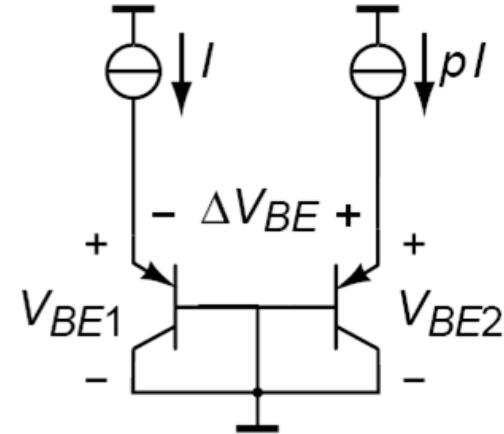
$$V_2 - V_1 = \frac{kT}{q} \ln \left(\frac{pI_1}{I_S} \right) - \frac{kT}{q} \ln \left(\frac{I_1}{I_S} \right) = \frac{kT}{q} \ln p.$$



اختلاف ولتاژهای بیس-امیترها نسبت به دما، خطی است.

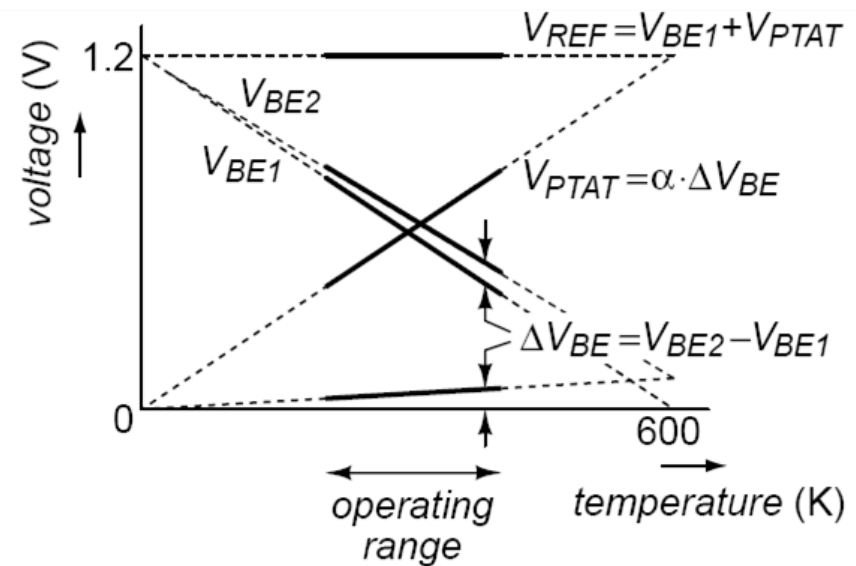


Table 7.6. Accuracy comparison of smart temperature sensors.

Reference	Inaccuracy	Range
LM75 [1]	$\pm 2.0^{\circ}\text{C}$	-25°C to 100°C
	$\pm 3.0^{\circ}\text{C}$	-55°C to 125°C
LM92 [17]	$\pm 0.33^{\circ}\text{C}$	at 30°C
	$\pm 1.5^{\circ}\text{C}$	-25°C to 150°C
DS1626 [18],	$\pm 0.5^{\circ}\text{C}$	0°C to 70°C
	$\pm 2.0^{\circ}\text{C}$	-55°C to 125°C
ADT7301 [19]	$\pm 1.0^{\circ}\text{C}$	0°C to 70°C
	$\pm 3.0^{\circ}\text{C}$	-40°C to 125°C
SMT160-30 [20]	$\pm 0.7^{\circ}\text{C}$	-30°C to 100°C
	$\pm 1.2^{\circ}\text{C}$	-45°C to 130°C